



BITS Pilani

Pilani | Dubai | Goa | Hyderabad

Computer Architecture (CS F342)

Upendra Singh, BITS Pilani



Computer Architecture Lab

Instructor: Upendra Singh
p20170428@pilani.bits-pilani.ac.in

TA1: ALARK FAJALIA
f20180296@pilani.bits-pilani.ac.in

TA2: AVADH RAJESH HARKISHANKA
f20180322@pilani.bits-pilani.ac.in

TA3: JVN Saketh Ram
h20200242@pilani.bits-pilani.ac.in

Section: P3 and P6

Day & Time: Tuesday, 10,11 hrs (P3)
Tuesday, 7,8 hrs (P6)

Reference Books: **“Verilog HDL: A guide to Digital Design and Synthesis”** by Samir Palnitkar.

Course Objectives



Getting started with HDL program using Icarus Simulator



Understand basic Verilog language primitives (e.g. module, data types, identifiers, vectors, registers, keywords etc.)



To understand the various types of modelling




BITS Pilani

Pilani | Dubai | Goa | Hyderabad

• Lab – 6

- Single Cycle Datapath Design

Single Cycle Datapath

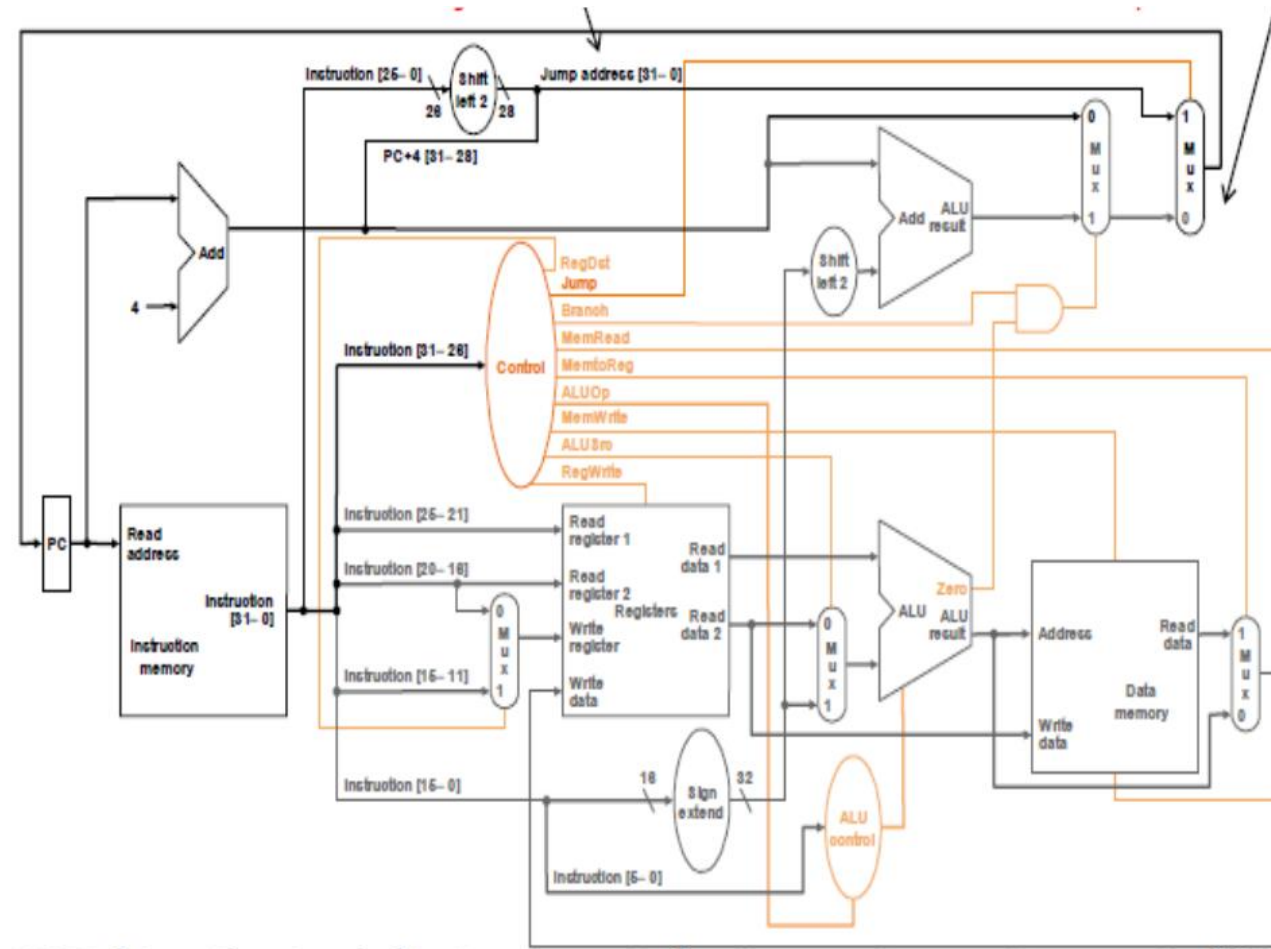

Single Cycle Datapath

- Datapath consists of the functional units of the processor.
 - Elements that hold data.
 - Program counter, register file, instruction memory, etc.
 - Elements that operate on data.
 - ALU, adders, etc.
 - Buses for transferring data between elements.
 - Control commands the Datapath regarding when and how to route and operate on data.

Single Cycle Datapath

- To showcase the process of creating a datapath and designing a control, we will be using a subset of the MIPS instruction set. Our available instructions include:
 - add, sub, and, or, slt
 - lw, sw
 - beq, j




Steps Taken to Execute a Program

- Now, we can talk about the general steps taken to execute a program.
 - Instruction fetching: use the address in the PC to fetch the current instruction from instruction memory.
 - Instruction decoding: determine the fields within the instruction
 - Instruction execution: perform the operation indicated by the instruction.
 - Update the PC to hold the address of the next instruction.

Steps Taken to Execute a Program

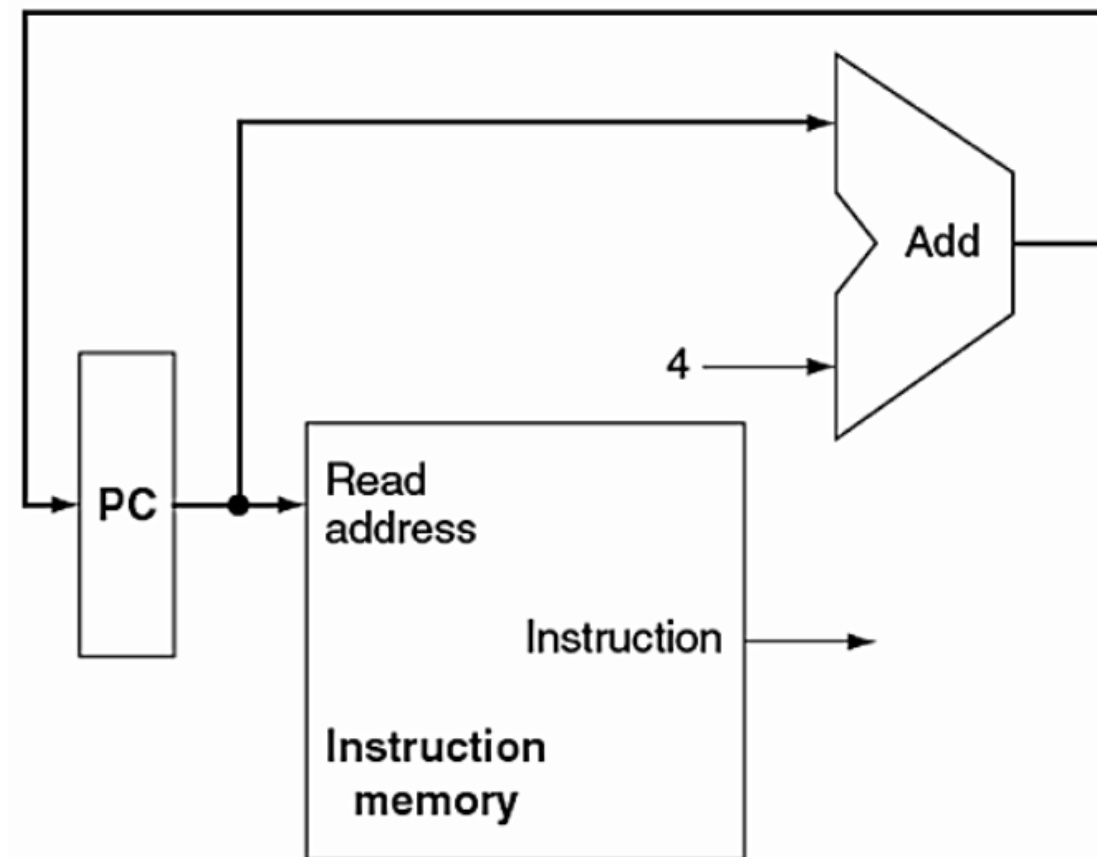- Fetch the instruction at the address in PC.
- Decode the instruction.
- Execute the instruction.
- Update the PC to hold the address of the next instruction.



Note: we perform PC+4 because MIPS instructions are word-aligned.

R-Format Instructions

- All R-format instructions read two registers, rs and rt, and write to a register rd.

Name	Fields					
Field Size	6 bits	5 bits	5 bits	5 bits	5 bits	6 bits
R format	op	rs	rt	rd	shamt	funct

op – instruction opcode.

rs – first register source operand.

rt – second register source operand.


rd – register destination operand.

shamt – shift amount.

funct – additional opcodes.


Datapath for R-format Instructions.

1. Grab instruction address from PC.

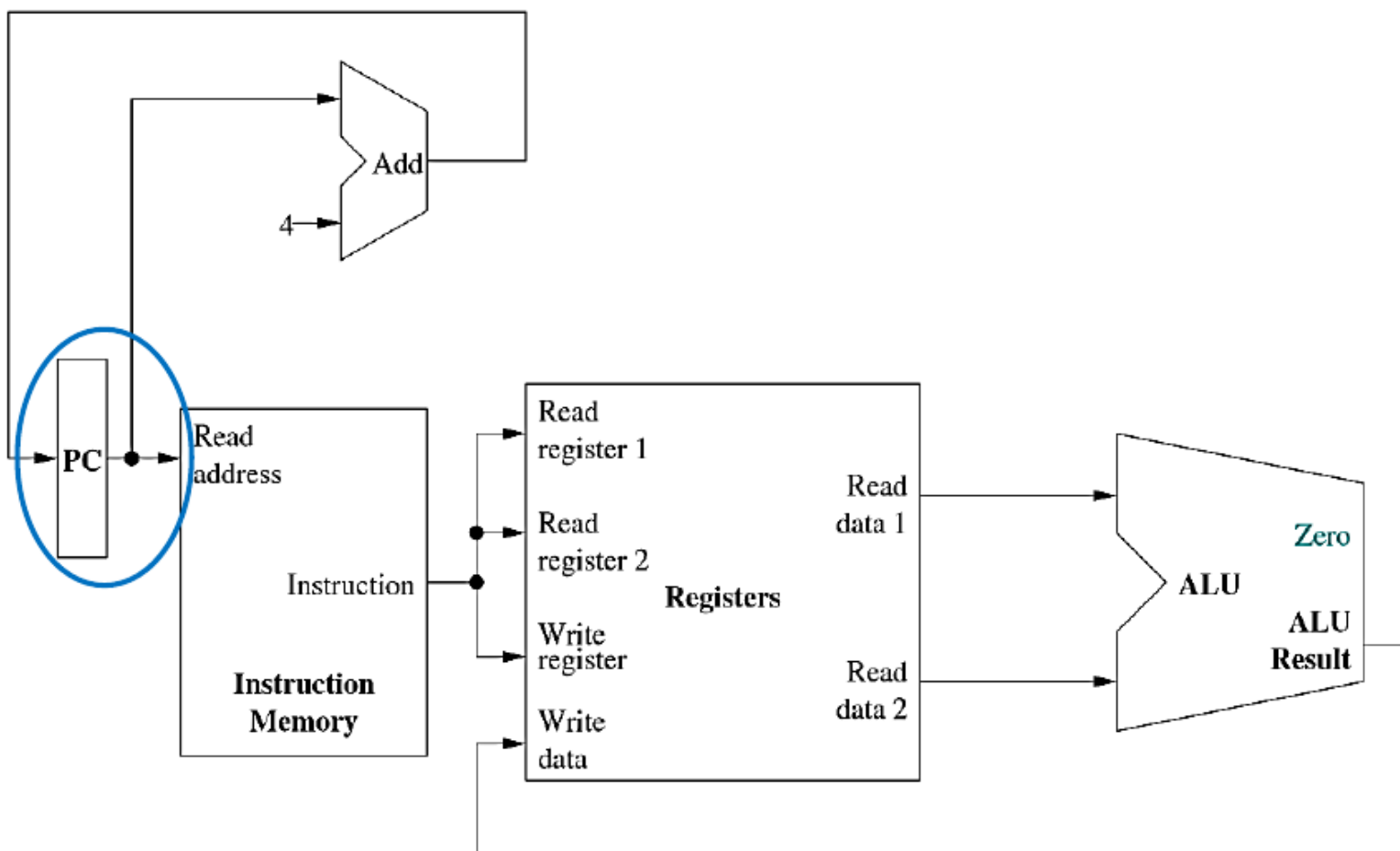


Datapath for R-format Instructions.

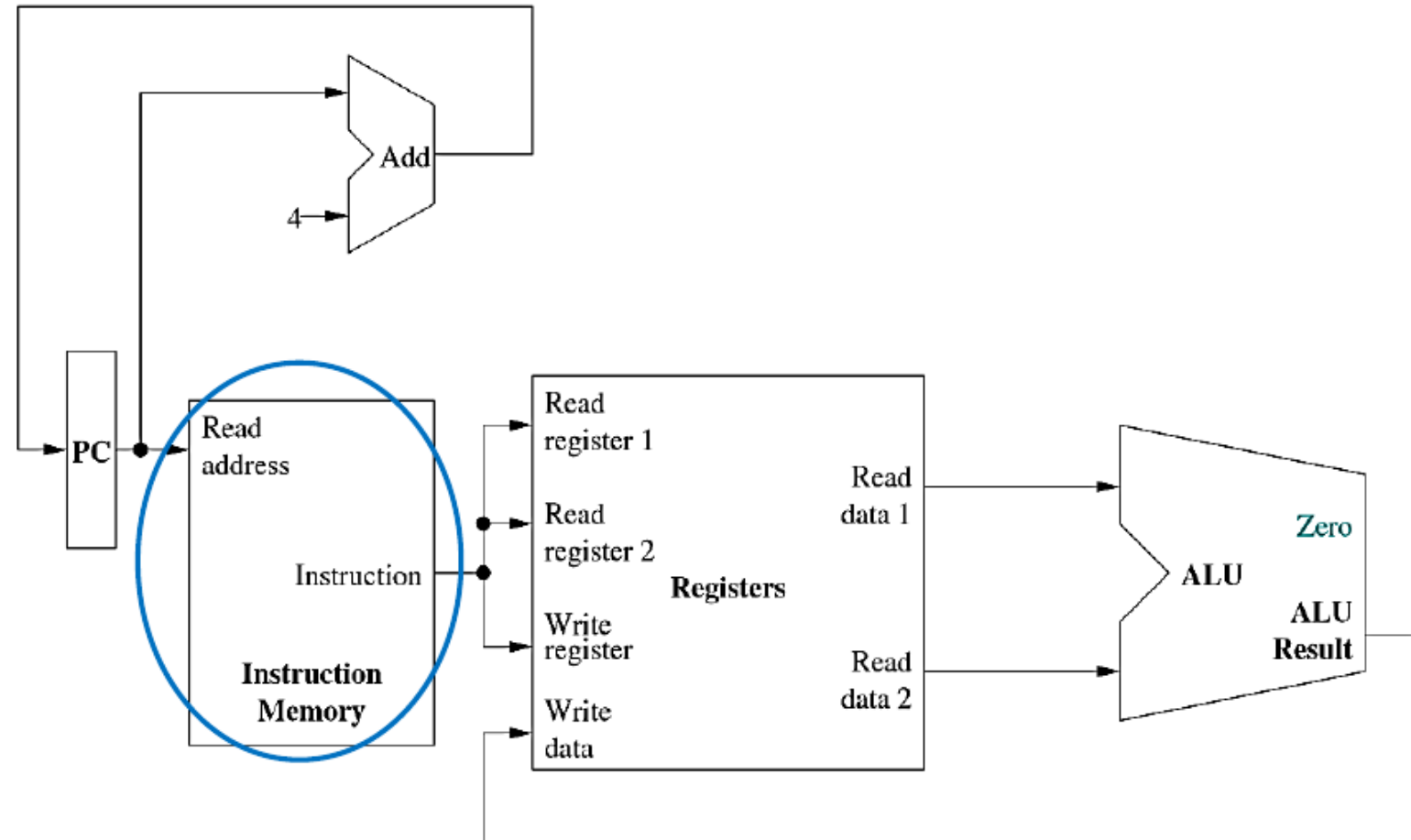2. Fetch instruction from instruction memory.
3. Decode instruction.




Datapath for R-format Instructions.

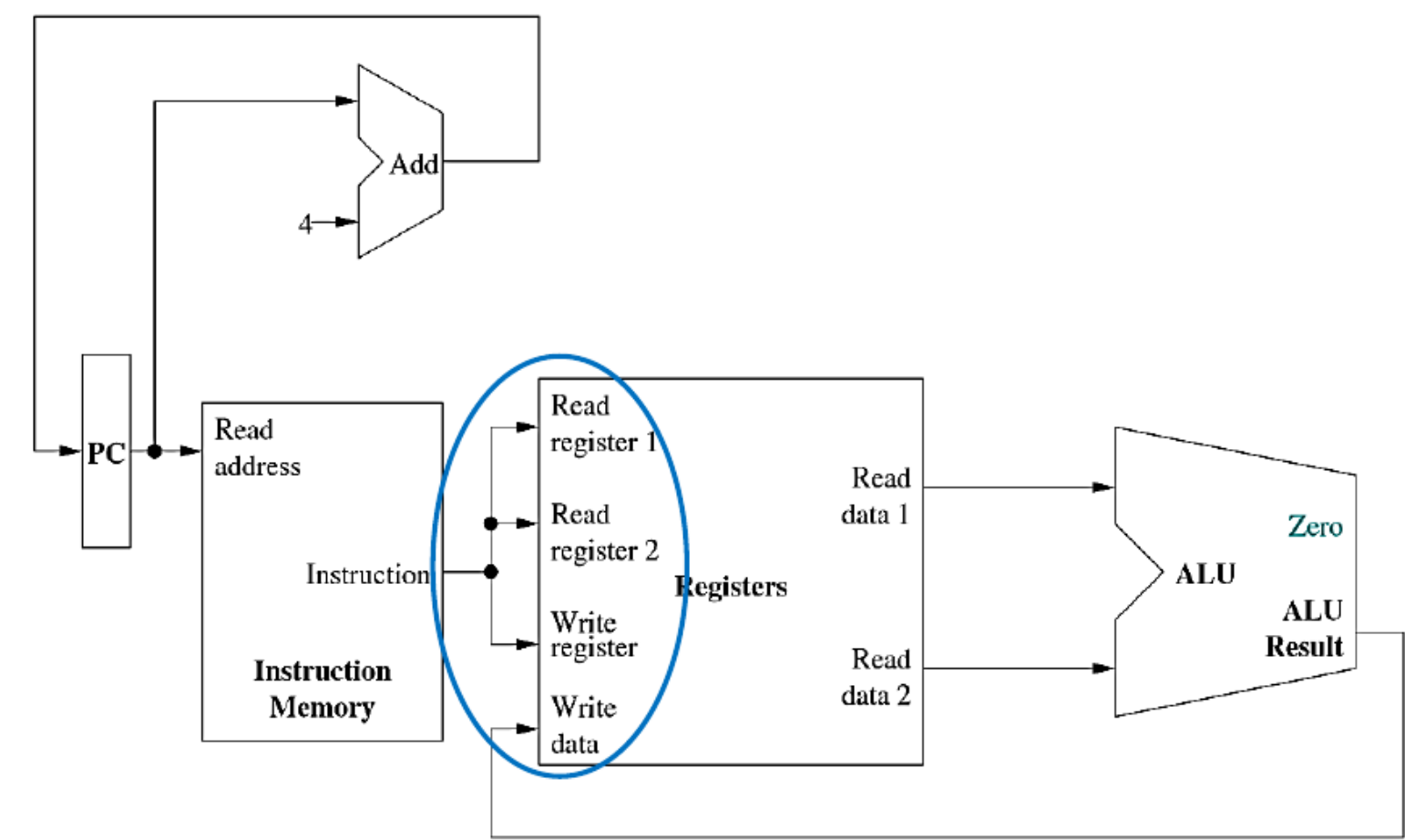4. Pass rs, rt, and rd into read register and write register arguments.




Datapath for R-format Instructions.

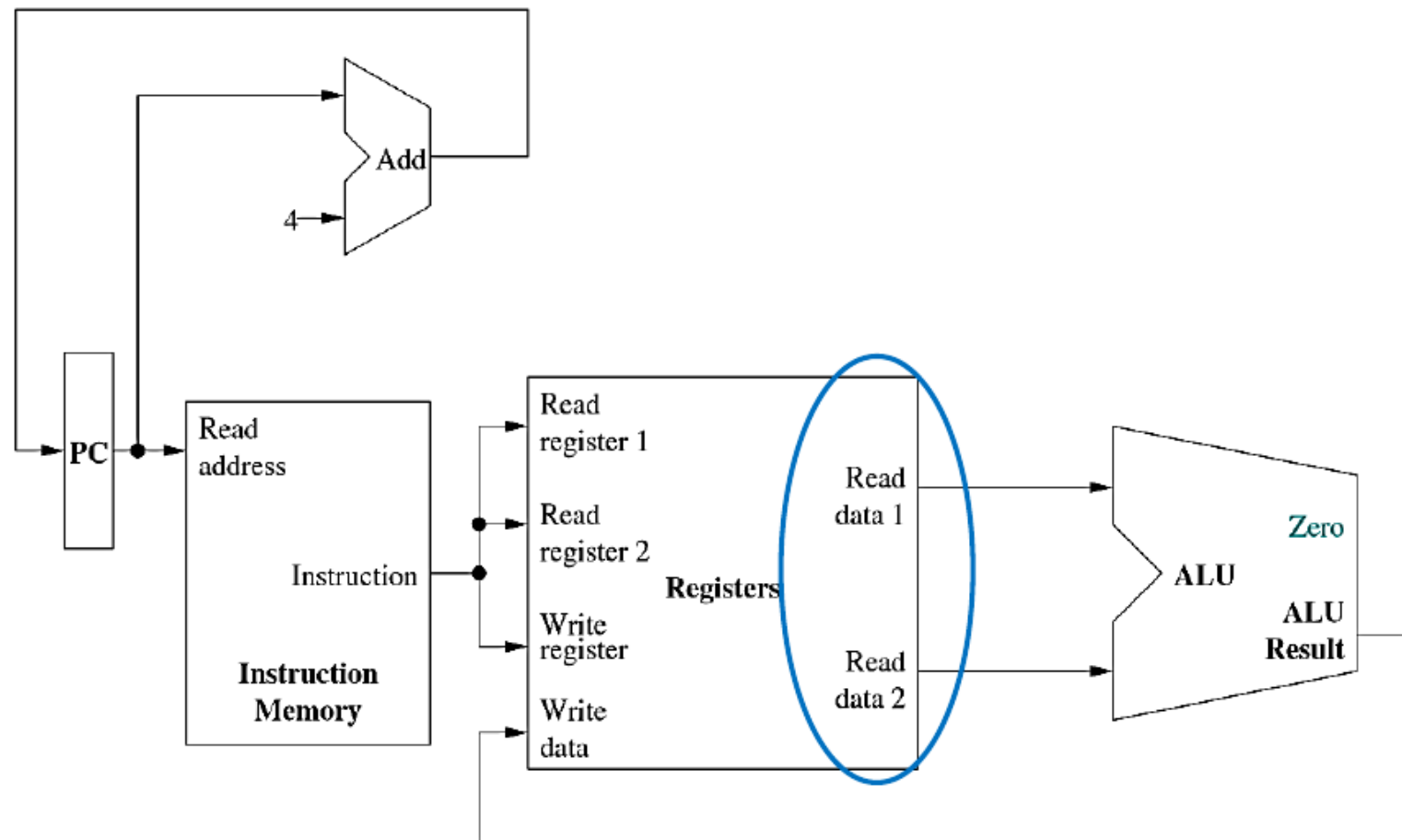5. Retrieve data from read register 1 and read register 2 (rs and rt).




Datapath for R-format Instructions.

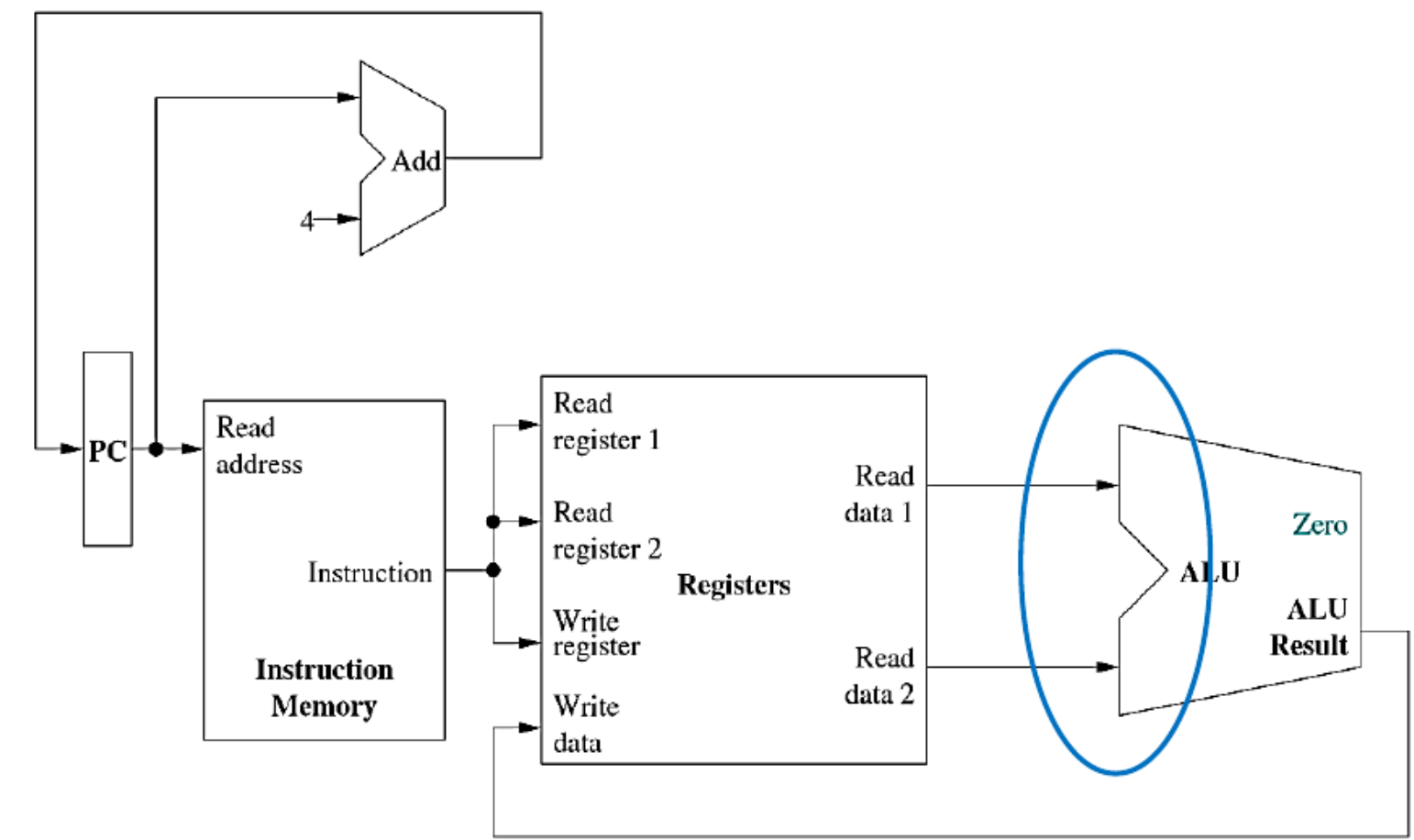6. Pass contents of rs and rt into the ALU as operands of the operation to be performed.




Datapath for R-format Instructions.

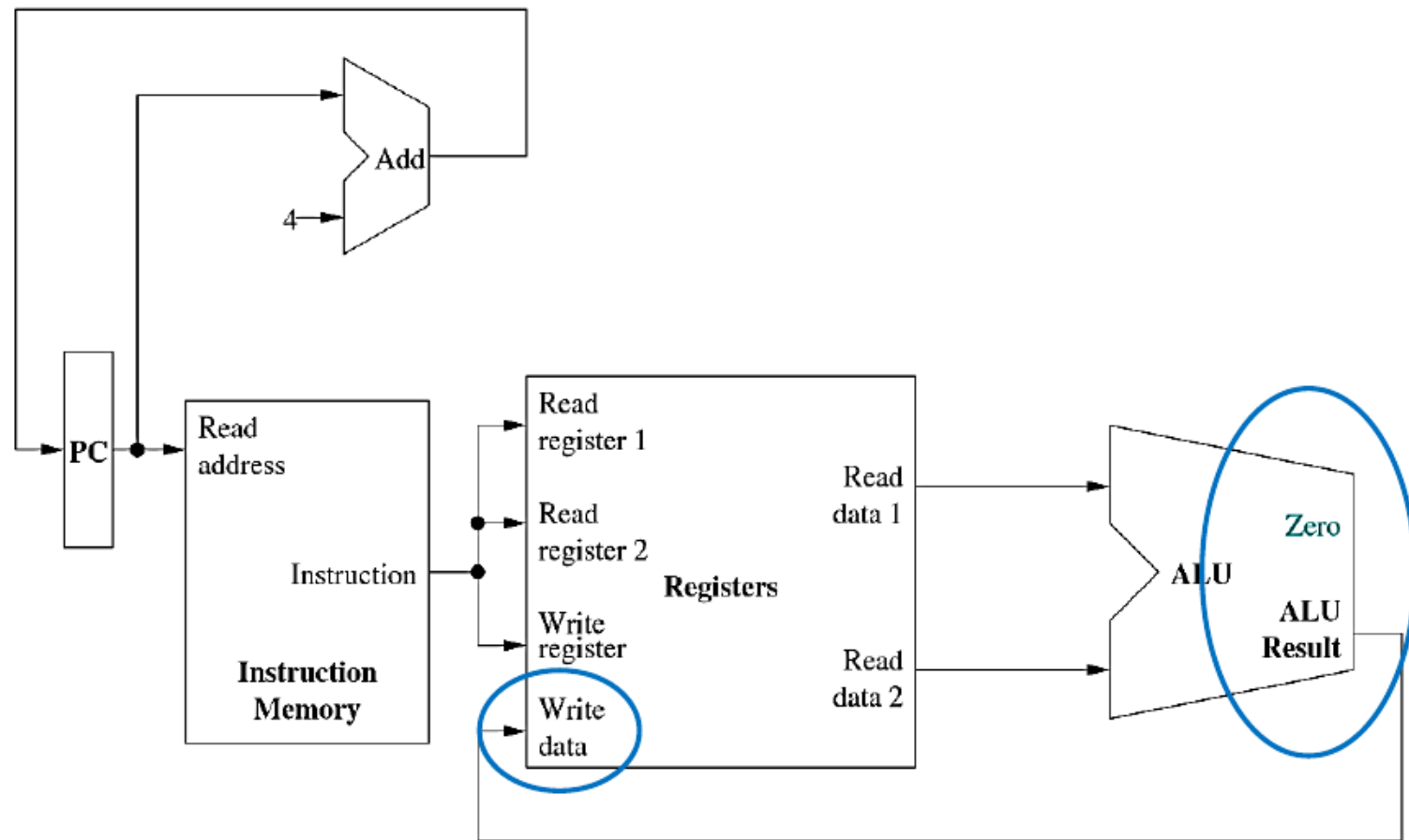7. Retrieve result of operation performed by ALU and pass back as the write data argument of the register file (with the RegWrite bit set).



Datapath for R-format Instructions.

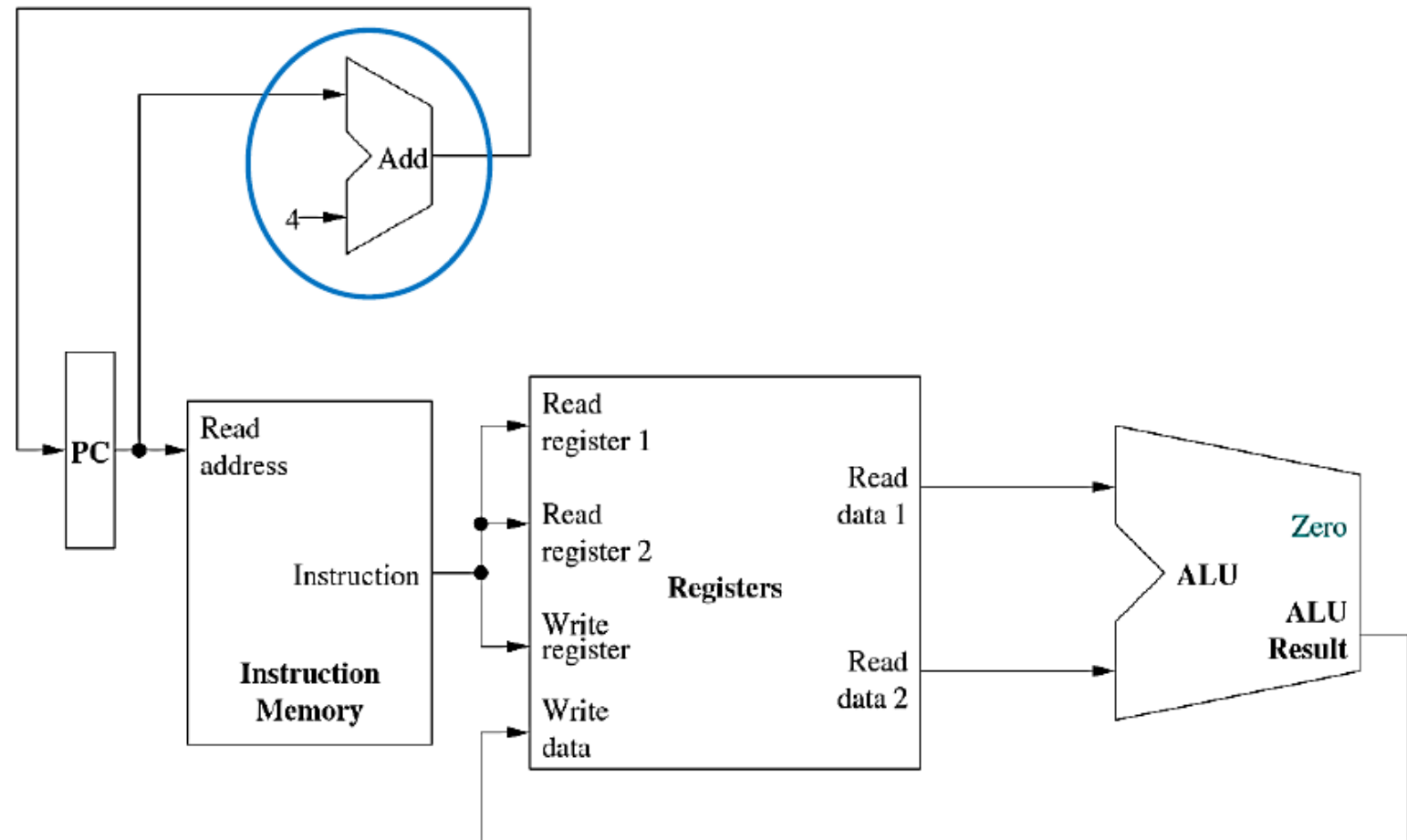8. Add 4 bytes to the PC value to obtain the word-aligned address of the next instruction.




Component list in SCD

Following are the hardware components

 - 1. Instruction Memory**
- 2. Register File (Lab 5)**
- 3. ALU (Lab 4)**
- 4. Control Unit and ALU Control (Lab 4)**
- 5. Data Memory**
- 6. Sign Extender**
- 7. Shifter (Lab 3)**
- 8. Program Counter**
- 9. Adders (required for computing next PC) (Lab 2)**
- 10. Multiplexers (Lab 1)**

Instruction Memory

- First, we have instruction memory.
 - Instruction memory is a state element that provides read-access to the instructions of a program and, given an address as input, supplies the corresponding instruction at that address.




Instruction Memory

```
module Instruction_Memory(Inst, PC, clock);
    input[31:0] PC;
    input clock;
    output[31:0] Inst;
    reg [31:0] memory [0:31];
    reg [31:0] Inst;
    integer addr;
    initial begin
        memory[0] = 32'b00000000000000000000000000000000; // nop
        memory[1] = 32'b00000000000000000000000000000000; // nop
        memory[2] = 32'b00000000000000000000000000000000; // nop
        memory[3] = 32'b10001100000010001000000000000100; // lw  $s1($17), 8($0)
        memory[4] = 32'b10001100000010010000000000000100; // lw  $s2($18), 4($0)
        memory[5] = 32'b000000010001100100100100000000010000; // add $t0($8), $s1($17), $s2($18)

        always @(posedge clock) begin
            addr = PC[31:0];
            Inst = memory[addr/4];
        end
    end
end
```

Program Counter

 - Next, we have the program counter or PC.
 - The PC is a state element that holds the address of the current instruction. Essentially, it is just a 32-bit register which holds the instruction address and is updated at the end of every clock cycle.
 - Normally PC increments sequentially except for branch instructions




Program Counter

```
module PC(count, clock, reset);  
    input        clock, reset;  
    output       [31:0] count;  
    reg  [31:0] count;  
    always @(posedge clock)  
        if(!reset)  
            count = count + 1;  
        else  
            count = 0;  
endmodule
```

FADDER32 (2 modules)

 - The adder is responsible for incrementing the PC to hold the address of the next instruction.
- It takes two input values, adds them together and outputs the result.




```

module FADDER32 (carry, sum, A, B, CarryIn);
    input [31:0] A, B;
    input CarryIn;
    output [31:0] sum;
    output carry;
    wire c1, c2, c3;
    FADDER8 mod1 (c1, sum[7:0], A[7:0], B[7:0], CarryIn);
    FADDER8 mod2 (c2, sum[15:8], A[15:8], B[15:8], c1);
    FADDER8 mod3 (c3, sum[23:16], A[23:16], B[23:16], c2);
    FADDER8 mod4 (carry, sum[31:24], A[31:24], B[31:24], c3);
endmodule
    
```


Register File

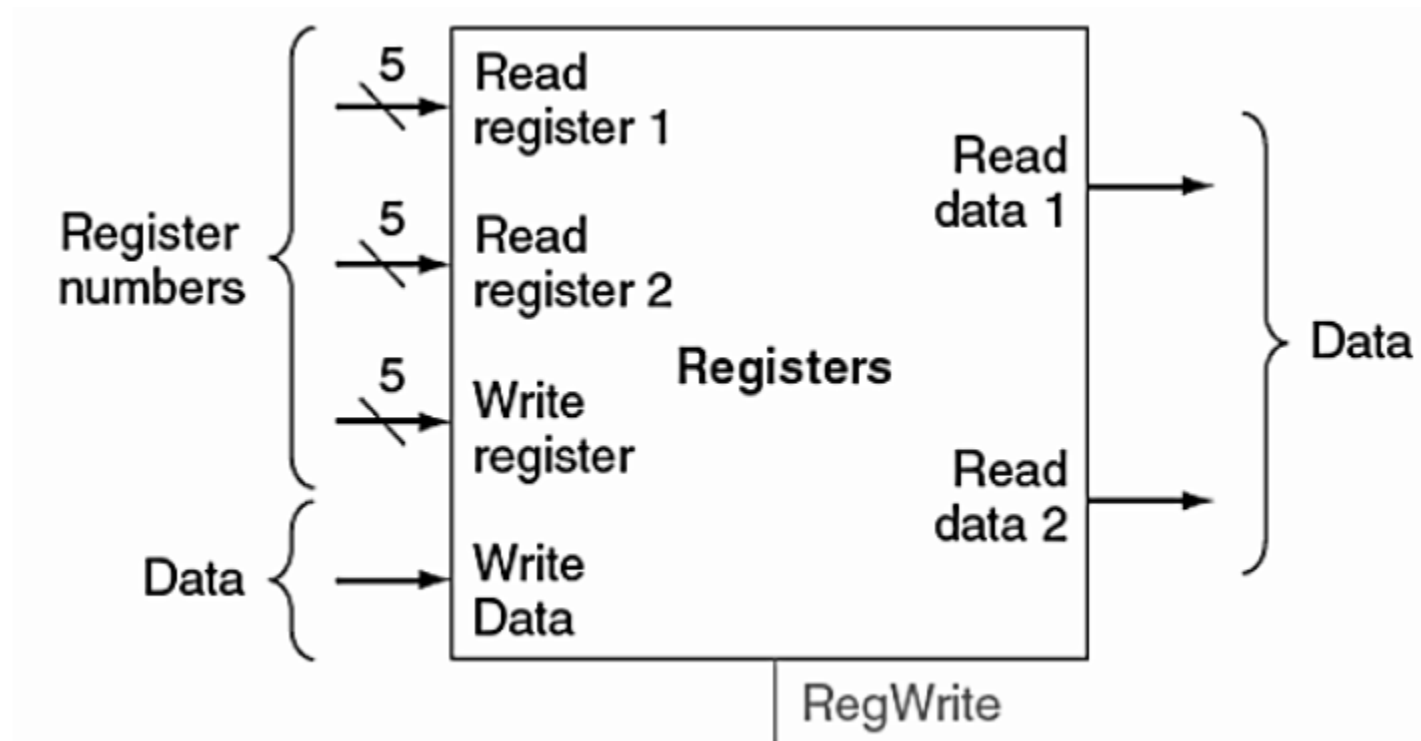- To support R-format instructions, we'll need to add a state element called a register file. A register file is a collection readable/writable registers.
- **Read register 1** – first source register. 5 bits wide.
- **Read register 2** – second source register. 5 bits wide.
- **Write register** – destination register. 5 bits wide.
- **Write data** – data to be written to a register. 32 bits wide.



Register File

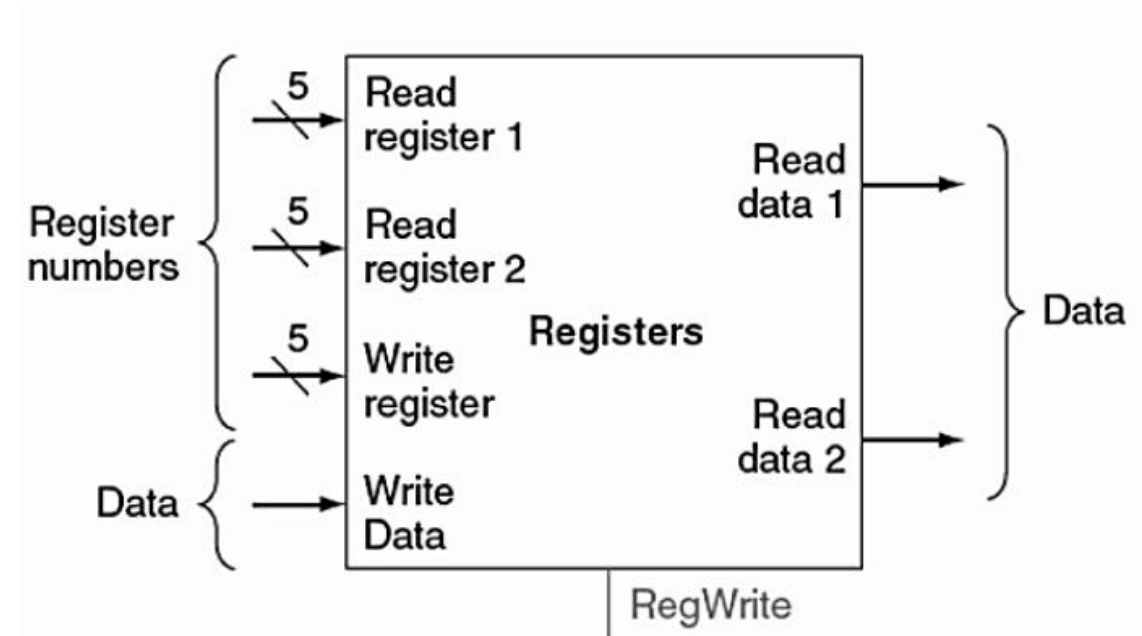- At the bottom, we have the RegWrite input. A writing operation only occurs when this bit is set.
- The two output ports are:
 - Read data 1 – contents of source register 1.
 - Read data 2 – contents of source register 2.



Register File

```
module d_ff(q, d, clock, reset);
```

```
    input d, clock, reset;
```

```
    output q;
```

```
    reg q;
```

```
    always @ (posedge clock or negedge reset)
```

```
    if(~reset)
```

```
        q = 1'b0;
```

```
    else
```

```
        q = d;
```

```
endmodule
```

```
module reg_32bit(q, d, clock, reset);
```

```
    input [31:0] d;
```

```
    input clock, reset;
```

```
    output [31:0] q;
```

```
    genvar j;
```

```
    generate
```

```
        for(j = 0; j < 32; j = j + 1) begin: d_loop
```

```
            d_ff ff(q[j], d[j], clock, reset);
```

```
        end
```

```
    endgenerate
```

```
endmodule
```


Register File

- Thirty two registers of 32-bit wide (32 instances)

```
reg_32bit r0 (w0, WriteData, c0, Reset);  
reg_32bit r1 (w1, WriteData, c1, Reset);  
reg_32bit r2 (w2, WriteData, c2, Reset);  
reg_32bit r3 (w3, WriteData, c3, Reset);
```

ALU Unit

 - To actually execute R-format instructions, we need to include the ALU element.
 - The ALU performs the operation indicated by the instruction.
 - It takes two operands, as well as a 4-bit wide operation selector value. The result of the operation is the output value.




ALU Unit

```
module ALU32Bit(Zero, CarryOut, Result, A, B, Op);
    input [2:0] Op;
    input [31:0] A, B;
    output [31:0] Result;
    reg [31:0] Result;
    output CarryOut, Zero;
    reg CarryOut;
    assign Zero = (({Result} == 0)) ? 1 : 0;
    always @ (Op, A, B) begin
        case(Op)
            0: Result <= A & B;
            1: Result <= A | B;
            2: {CarryOut, Result[31:0]} <= A + B;
            6: {CarryOut, Result[31:0]} <= A - B;
            7: Result <= A < B ? 1 : 0;
            default: Result <= 0;
        endcase
    end
endmodule
```

Data Memory

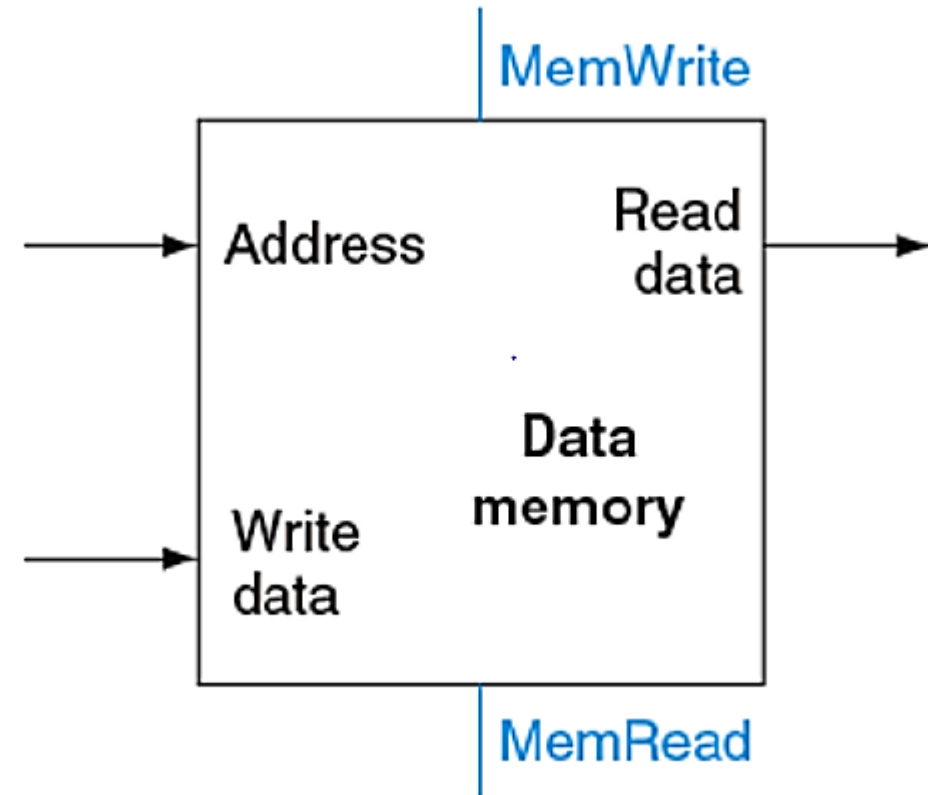- There are two inputs. One for the address of the memory location to access, the other for the data to be written to memory if applicable.
- The output is the data read from the memory location accessed, if applicable.



Data Memory

- **Input:-** Read address, write address, write data

- **Output:** Read data
- ```

input MemRead, MemWrite, Clock;
input [31:0] ReadAddress, WriteAddress;
input [31:0] WriteData;
output reg [31:0] ReadData;
reg [31:0] memory [0:31];
integer raddr, waddr;

```

```

initial begin

```

```

 memory[0] = 32'b00; // nop
memory[1] = 32'b0000000000000000000000000000000001010100; // Value of 84
memory[2] = 32'b00000000000000000000000000000000000001011; // Value of 11

```

# Data Memory

```
always @(posedge Clock) begin
 raddr = ReadAddress;
 waddr = WriteAddress;
 if (MemRead)
 ReadData = memory[raddr/4];
 else if (MemWrite)
 memory[waddr/4] = WriteData;
end
```



# Multiplexers

---

- Multiplexers 32bit-2x1 (4 modules)
  - Generating the new address after the branch MUX
  - Generating the new address after the Jump MUX
  - Writing back to register file
  - Selecting the second ALU Source
- Multiplexers 5bit-2x1 (1 module)
  - Selecting the writing register

# Multiplexers 5bit-2x1

```
module MUX5Bit_2To1(out, select, q1, q2);
 input [4:0] q1, q2;
 input select;
 output [4:0] out;
 genvar j;
 generate for(j = 0; j < 5; j = j + 1)
 begin: mux_loop
 Mux2To1 Mux(out[j], select, q1[j], q2[j]);
 end
endgenerate
endmodule
```




# Multiplexers 32bit-2x1

```
module Mux32Bit_2To1(out, select, in1, in2);
 input [31:0] in1, in2;
 input select;
 output [31:0] out;
 Mux8Bit_2To1_generate Mux1(out[7:0], select, in1[7:0], in2[7:0]);
 Mux8Bit_2To1_generate Mux2(out[15:8], select, in1[15:8], in2[15:8]);
 Mux8Bit_2To1_generate Mux3(out[23:16], select, in1[23:16], in2[23:16]);
 Mux8Bit_2To1_generate Mux4(out[31:24], select, in1[31:24], in2[31:24]);
endmodule
```
 
# Sign Extender

- To perform sign-extending, we can add a sign extension element.
  - The sign extension element takes as input a 16-bit wide value to be extended to 32-bits.
  - To sign extend, we simply replicate the most-significant bit of the original field until we have reached the desired field width.



# Sign Extender

- Sign Extend the Branch Offset

```
module Sign_Extender(out, in);
 input [15:0] in;
 output [31:0] out;
 assign out = { {16{in[15]}} , in};
endmodule
```

# Shifter (2 Modules)

- Shift left by 2 bits the Sign Extended **Branch Offset**
- Shift left by 2 bits the **Jump Offset**.

```
module Shift_Left(out, in);
 input [31:0] in;
 output [31:0] out;
 assign out = {in[29:0], 1'b0, 1'b0};
endmodule
```

# Concatenate PC and Jump Offset

- Concatenate PC and Left Shifted Jump Offset

```
module concatJuPC(out, J, PC);
 input [31:0] J, PC;
 output [31:0] out;
 assign {out} = {{PC[31:28]}, {J[27:0]}};
endmodule
```

# ALU Control Unit

```
module ALUControlUnit(Op, Func, ALUOp);
 input [5:0] Func;
 input [1:0] ALUOp;
 output [2:0] Op;
 assign Op[0] = ALUOp[1] & (Func[3] | Func[0]);
 assign Op[1] = (~ALUOp[1]) | (~Func[2]);
 assign Op[2] = ALUOp[0] | (ALUOp[1] & Func[1]);
endmodule
```



# Main Control Unit

- Generate the Control Signals

```
output RegDst, Jump, ALUSrc, MemToReg, RegWrite, MemRead, MemWrite,
 Branch, ALUOp0, ALUOp1;
input [5:0] Op;
wire RFormat, LW, SW, BEQ, J;
assign RFormat = (~Op[5]) & (~Op[4]) & (~Op[3]) & (~Op[2]) & (~Op[1]) & (~Op[0]);
assign LW = (Op[5]) & (~Op[4]) & (~Op[3]) & (~Op[2]) & (Op[1]) & (Op[0]);
assign SW = (Op[5]) & (~Op[4]) & (Op[3]) & (~Op[2]) & (Op[1]) & (Op[0]);
assign BEQ = (~Op[5]) & (~Op[4]) & (~Op[3]) & (Op[2]) & (~Op[1]) & (~Op[0]);
assign J = (~Op[5]) & (~Op[4]) & (~Op[3]) & (~Op[2]) & (Op[1]) & (~Op[0]);
```



# Final Task

---

- Integrate all Modules.
- Test on given testbench.



---

# Thank You